



geradores

elétrico

ideal

lei de Pouillet

potência máxima útil

$$V = \mathcal{E} - r_{int} \cdot i$$

$$i = \frac{\mathcal{E}}{r_{int} + R}$$

$$P_{m\acute{a}x} = \frac{\mathcal{E}^2}{4 \cdot r}$$