

AULA 18

Corrente / Resistência

- 146 – E
- 147 – C
- 148 – D
- 149 – E
- 150 – B
- 151 – E
- 152 – B
- 153 – E
- 154 – C
- 155 – A
- 156 – C
- 157 – E
- 158 – C
- 159 – E
- 160 – D
- 161 – D
- 162 – D
- 163 – C
- 164 – B
- 165 – A
- 166 – D
- 167 – E
- 168 – A
- 169 – C
- 170 – A
- 171 – B
- 172 – E
- 173 – B
- 174 – D
- 175 – A
- 176 – D
- 177 – A
- 178 – C
- 179 – D
- 180 – B
- 181 – E
- 182 – A
- 183 – C
- 184 – C
- 185 – E
- 186 – E
- 187 – E
- 188 – E
- 189 – A
- 190 – A

AULA 19

Resistores

- 191 – A
- 192 – B
- 193 – D
- 194 – E
- 195 – C
- 196 – E
- 197 – C
- 198 – B
- 199 – A
- 200 – B
- 201 – D
- 202 – D
- 203 – C
- 204 – C
- 205 – B
- 206 – A
- 207 – E
- 208 – B
- 209 – E
- 210 – A
- 211 – C
- 212 – C
- 213 – D
- 214 – D
- 215 – D
- 216 – A
- 217 – C
- 218 – C
- 219 – B
- 220 – D
- 221 – C
- 222 – B
- 223 – D
- 224 – B
- 225 – A
- 226 – B
- 227 – C
- 228 – E
- 229 – E
- 230 – A
- 231 – C
- 232 – E
- 233 – B
- 234 – D
- 235 – B

AULA 20

Associação de Resistores

- 236 – A
- 237 – D
- 238 – B
- 239 – D
- 240 – A
- 241 – A
- 242 – D
- 243 – C
- 244 – E
- 245 – E
- 246 – D
- 247 – B
- 248 – E
- 249 – E
- 250 – A
- 251 – B
- 252 – B
- 253 – B
- 254 – C
- 255 – C
- 256 – D
- 257 – E
- 258 – E
- 259 – E
- 260 – E
- 261 – E
- 262 – E
- 263 – D
- 264 – A
- 265 – D
- 266 – D
- 267 – A
- 268 – B
- 269 – C
- 270 – B
- 271 – D
- 272 – B
- 273 – C
- 274 – A
- 275 – D
- 276 – A
- 277 – D
- 278 – D
- 279 – E
- 280 – A

AULA 21

Circuitos Elétricos

- 281 – C
- 282 – A
- 283 – C
- 284 – E
- 285 – D
- 286 – C
- 287 – E
- 288 – A
- 289 – D
- 290 – D
- 291 – D
- 292 – E
- 293 – B
- 294 – A
- 295 – D
- 296 – C
- 297 – C
- 298 – B
- 299 – D
- 300 – E
- 301 – A
- 302 – B
- 303 – C
- 304 – A
- 305 – B
- 306 – B
- 307 – D
- 308 – B
- 309 – B
- 310 – B
- 311 – 10 = 2+8
- 312 – B
- 313 – C
- 314 – C
- 315 – C
- 316 – B
- 317 – B
- 318 – E
- 319 – 56 = 8+16+32
- 320 – E
- 321 – E
- 322 – C
- 323 – E
- 324 – C
- 325 – A

AULA 22

Geradores

- 326 – D
- 327 – D
- 328 – C
- 329 – C
- 330 – A
- 331 – B
- 332 – C
- 333 – D
- 334 – E
- 335 – E
- 336 – E
- 337 – B
- 338 – A
- 339 – E
- 340 – B